

**CSE 350**  
**Spring 2024**  
**Quiz 04**

**Total Marks: 20**

**Time: 15 minutes**

Name:	St. ID:	Section:	Serial Number (From the Attendance Sheet)

You have to send a confidential voice message (analog signal) to your friend via an optical fiber. For this, first, you have to convert your message (into a digital signal) so that it can be transmitted through the fiber. The **maximum and minimum values of your original message are 0V and +10V, respectively**. Your friend has a digital signal receiver that can handle a **maximum of 2% of quantization error** and has a **binary-weighted DAC circuit** (where,  $R = 20 \text{ k}\Omega$ ,  $R_F = 10 \text{ k}\Omega$ , and  $V_{ref} = -10\text{V}$ ) to convert the received digital signal into an analog signal.

**Q#1.[CO3]** Calculate the **minimum number of bits** required in this case. [5]

**Q#2.[CO3]** Calculate the **number of resistors** required in this case if you use a **flash ADC** circuit. [5]

**Q#3.[CO3]** Calculate the **number of OP-AMPs** required in this case if you use a **flash ADC** circuit. [5]

**Q#4.[CO3]** If your friend receives **01101**, what will be the value of the **converted analog signal in voltage**? [5]

2.1

$$\% \text{ of quantization error} = \frac{\Delta Q}{|V_{max} - V_{min}|} \times 100$$

$$2 = \frac{\Delta Q}{|V_{max} - V_{min}|} \times 100$$

$$N = 4.64$$

$$\therefore \boxed{N = 5}$$

$$\Delta Q = \frac{1}{2} \Delta \quad [\Delta Q = \text{quantization error}]$$

$$\Delta = \frac{V_{max} - V_{min}}{L} \quad [\Delta = \text{resolution}]$$

$$L = 2^N \quad [L = \text{number of levels}]$$

$$N = \text{number of bits}$$

# Q.2

For flash ADC

$$\# \text{ Resistor} = 2^N = 2^5 = \boxed{32}$$

# Q.3

$$\# \text{ op-amp} = (2^N) - 1 = 2^5 - 1 = \boxed{31}$$

# Q.4

for DAC,

$$V_o = -V_{ref} \times \frac{R_f}{R} \left[ b_5 + \frac{b_4}{2} + \frac{b_3}{4} + \frac{b_2}{8} + \frac{b_1}{16} \right]$$

$$= -(-10) \times \frac{10}{20} \left[ 0 + \frac{1}{2} + \frac{1}{2} + 0 + \frac{1}{16} \right]$$

$$\Rightarrow \boxed{V_o = 4.0625V}$$

$$\left[ \begin{array}{l} b_5 = \text{MSB} \\ b_1 = \text{LSB} \end{array} \right]$$